
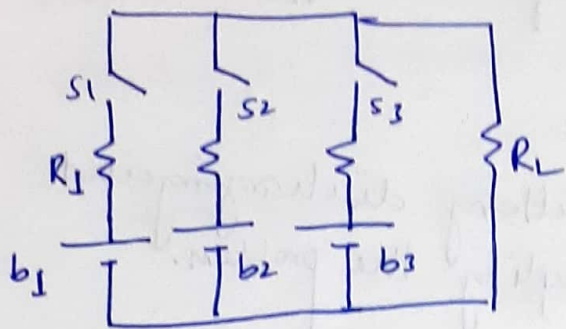


BATTERY BALANCING

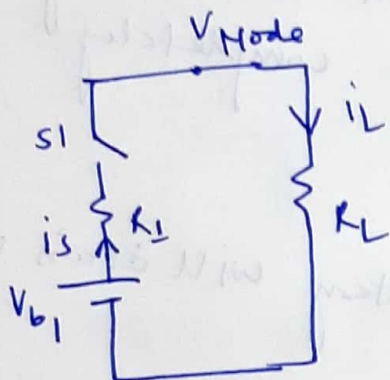


Let's Consider a simplified circuit to understand the concept of effective Resistance.



Let's Assume we want Node voltage to be constant at V_{Node} volts then the current coming out of the battery would be

$$\frac{V_{b1} - V_{Node}}{R_1} \rightarrow \text{When switch is closed}$$
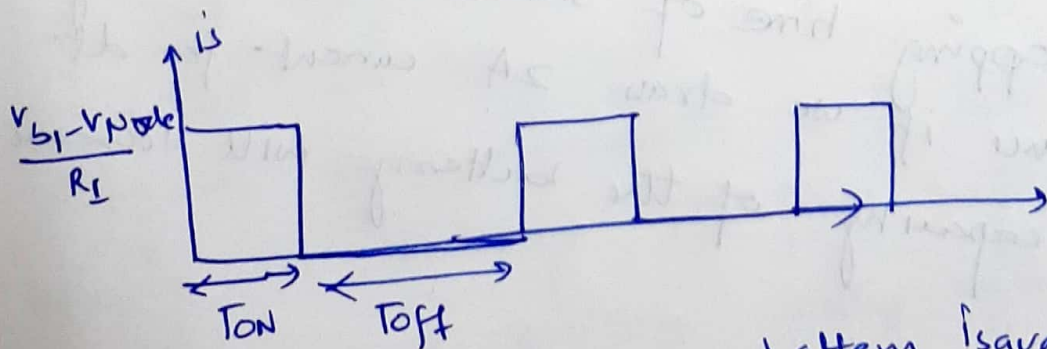
$$0 \rightarrow \text{When switch is closed}$$



Average current Delivered by battery $i_{Savg} = \left(\frac{T_{on}}{T_{on} + T_{off}} \right) \times \frac{V_b - V_{Node}}{R_1}$

duty cycle

$$\therefore i_{Savg} = d \times \frac{V_b - V_{Node}}{R_1} \text{ or } \frac{V_b - V_{Node}}{R_1/d}$$

effective Resistance seen by the Load

Hence we can say that by setting the switching frequency of the switch we can vary the effective resistance of the circuit.

→ Same concepts selected to the battery discharging and same assumptions made to simplify the problem.

Suppose battery capacity is given as 5Ah (Ampere hours)
⇒ If 5A current is drawn from the battery then it will take 1 hour to completely discharge it.

Hence if 2A is drawn then the battery will drain in

5A	→	1 hr
2A	→	$\frac{5}{2}$ hrs


Assuming stepping time of simulation to be very small Δt then if we draw 2A current for Δt time then capacity of the battery will decrease from

$$5 - \frac{5}{2} \times \Delta t \text{ A hr}$$

$$\text{percentage of battery remaining} = \frac{5 - \frac{5}{2} \times \Delta t}{5} \times 100$$

Remaining capacity

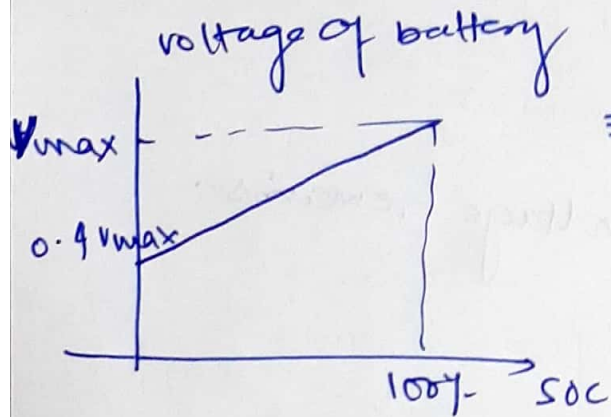Now, there is a concept of SOC (State of charge)
 There is a Relationship between voltage of battery
 & SOC ~~where~~ which we are assuming here to be
 Linear.



$\Rightarrow \text{eqn}$

$$V = V_{\max} \left(\frac{\text{SOC} \times 0.6}{100} + 0.4 \right)$$

→ SOC can be considered as Battery capacity only
 have in our case & capacity remaining is (SOC)

$$\left(5 - 5/2 \times dt / 5 \right) \times 100$$

$$\therefore V = V_{\max} \left(\frac{\left[\left[5 - 5/2 \times dt \right] / 5 \right] \times 100 \times 0.6}{100} + 0.4 \right)$$

Process followed:-

Which ever cell has max voltage, we will discharge it first.

suppose B1 14.3
More

B2: 12.3

B3: 11.6

so discharge it such as Node voltage remains whatever we need.

$$i_{avg} = \frac{V_b - V_{Node}}{R/d} = \frac{V_{Node}}{R_L}$$

eg. $d \left(\frac{14.3 - 8^{(say)}}{2^{say}} \right) = \frac{8}{100}^{(say)}$

$\therefore d = 0.025 \leftarrow$ This duty cycle must be kept?

so at any instant of time only 1 cell will be connected to the circuit and after dt (stepping time) algorithm will evaluate which cell has max voltage hence will discharge it first by connecting it to the circuit and setting duty cycle of the switch such that we get the Required Node voltage.